

# ECE 385 – Digital Systems Laboratory

Lecture 3 – Debugging TTL, Lab 3 Introduction  
Zuofu Cheng

Spring 2019

[Link to Course Website](#)




## Experiment 3 – Serial Logic Processor

- Design a 4-bit serial logic processor
- Performs 1 of 8 logical operations on 4-bit words (1 bit at a time, serially)
- All logical operations may be performed bit-wise with no additional storage
- Two 4-bit registers (A, B) which can serve as source/destination of each instruction
- Executes **single** instruction per EXECUTE signal

# Experiment 3 – Serial Processing

- All 8 operations (AND, OR, XOR, '1', NAND, NOR, XNOR) can be done bitwise
- Example of 8-bit bitwise addition (we won't need to implement this because it requires extra flip-flop for carry)

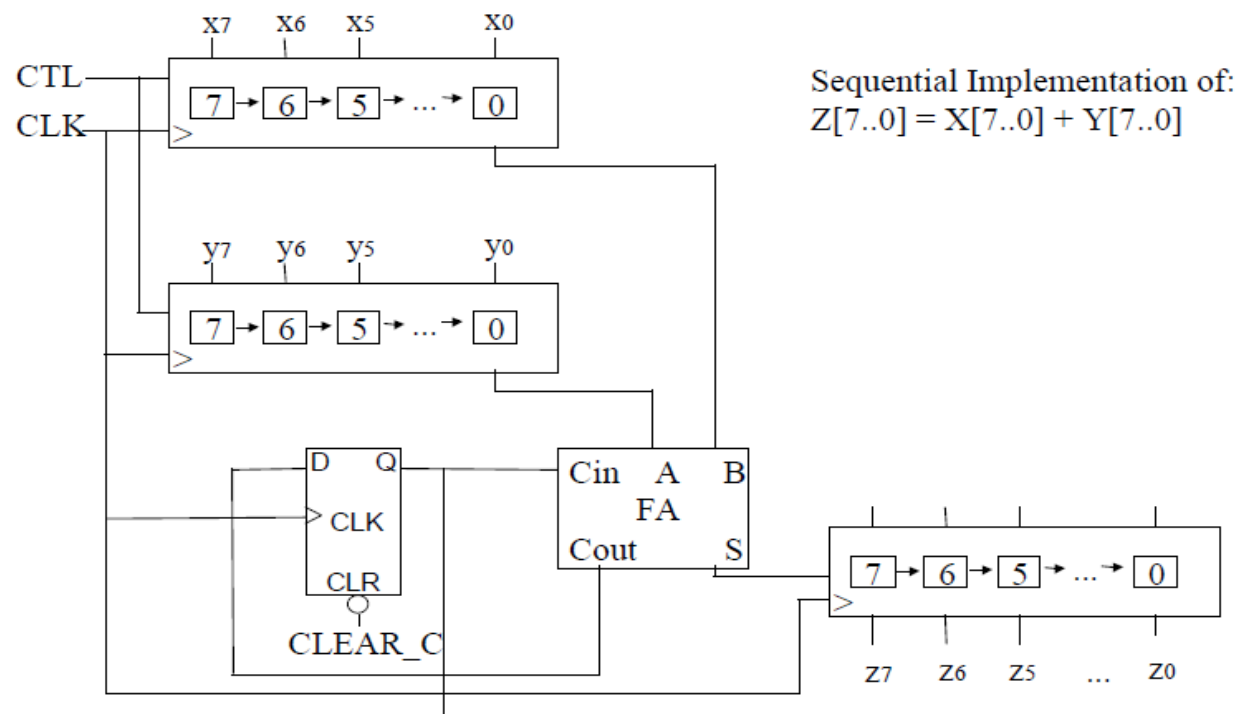
## Shift Register Applications Example: 8-Bit Serial Adder



# Experiment 3 – a 4-bit Serial Logic Processor
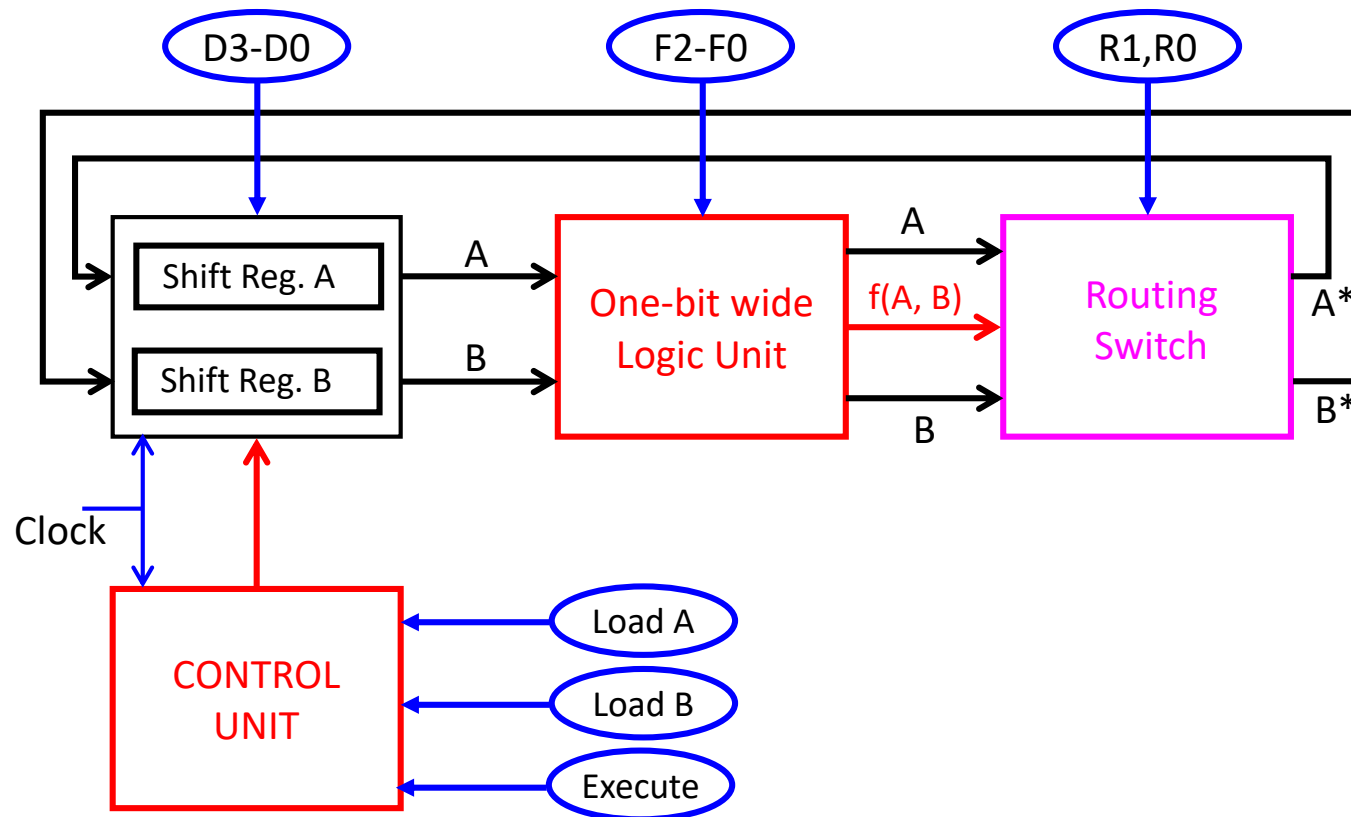
# Experiment 3 – Introduction & Goals

- A Bit-Serial Logic Processor
  - Two 4-bit registers A, B
  - A or B also serve as a destination register.
    - E.g., `AND A, B, A` /\* A AND B => A \*/



# Experiment 3 – Instructions and Design

- 8 Logic functions need to be implemented in the computation unit; function output routed appropriately
- Instructions specified by inputs D[3:0], F[2:0], R[1,0], LoadA, LoadB
- Single instruction executed on EXEC (CPU halts after execution of one instruction until EXEC is high during RE)

Function Selection Inputs			Computation Unit Output
F2	F1	F0	f(A, B)
0	0	0	A AND B
0	0	1	A OR B
0	1	0	A XOR B
0	1	1	1111
1	0	0	A NAND B
1	0	1	A NOR B
1	1	0	A XNOR B
1	1	1	0000


Routing Selection		Router Output	
R1	R0	A'	B'
0	0	A	B
0	1	A	F
1	0	F	B
1	1	B	A

## Experiment 3 – Register File

- Use two shift registers (as per Lab 2)
  - Use the parallel in capability (parallel load of D3-D0)
  - Use the parallel out capability (for debugging and demo)
  - Shift out only when EXECUTE is flipped on (and only process a 4-bit word)
  - Shift in from the output of the router
  - Clock input from the function generator (or switch for debugging)
    - We will test at 1 kHz as per Lab 2
  - Do not gate clock. But do not continuously shift either, will need to have control unit control mode pin.
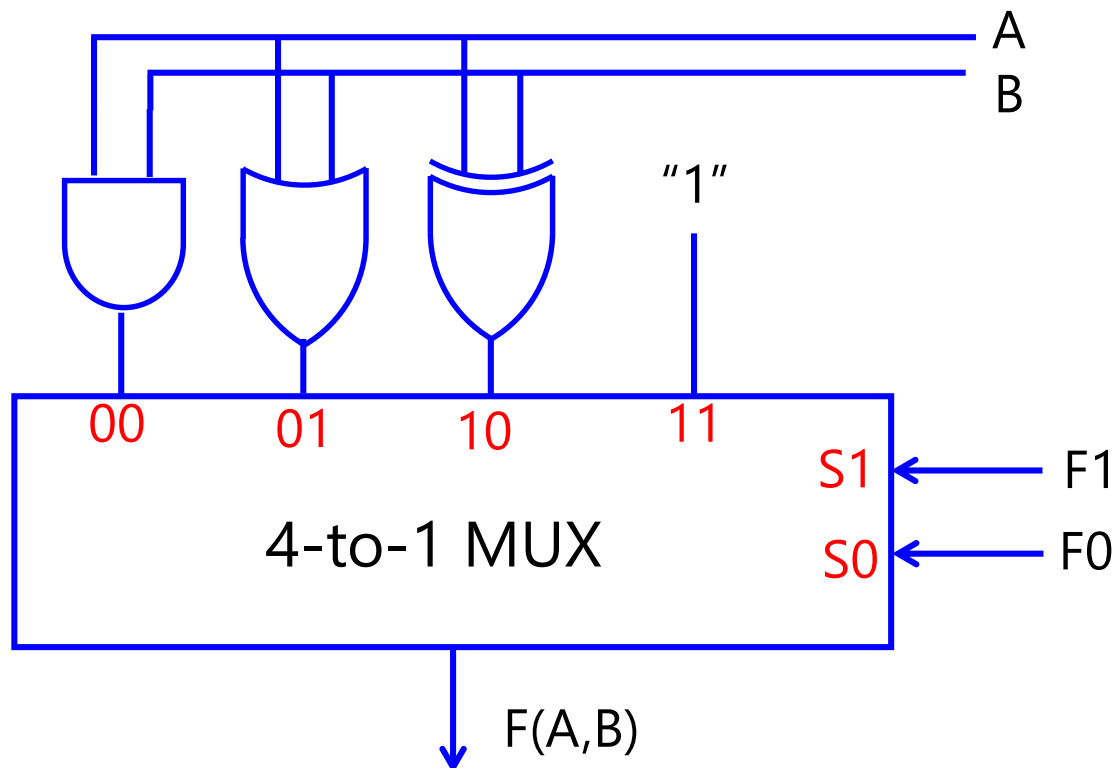
## Experiment 3 – Logic Unit

- Will need 8-1 MUX to implement 8 functions
- Example (half of what you will need)




Function Select F1,F0	Function Output F(A,B)
0 0	$A \cdot B$
0 1	$A + B$
1 0	$A \oplus B$
1 1	"1"


 
## Experiment 3 – Routing Unit

- Routes output of logic unit  $f(A,B)$  back to register file



Source Select $R1, R0$	Destination $A^*$	Destination $B^*$
0 0	$A$	$B$
0 1	$A$	$f(A, B)$
1 0	$f(A, B)$	$B$
1 1	$B$	$A$


This switch can be implemented using just two 4-to-1 Multiplexers!

## Experiment 3 – Control Unit

- This is the most challenging part of this design
  - When EXECUTE switch is ON, the controller starts the execute cycle and completes **exactly One Logic Instruction**. It then Halts. The Controller will not start another execution cycle until the EXECUTE switch is OFF and then ON again.
  - The controller also provides the Shift signals to the shift registers for an appropriate number of times to complete one execution cycle
    - Should be designed as a state machine (Mealy or Moore)
    - Controller must execute to completion regardless of subsequent changes to EXECUTE once cycle started
    - Could enumerate each count as separate state, but would require more states


# Experiment 3 – State Machine
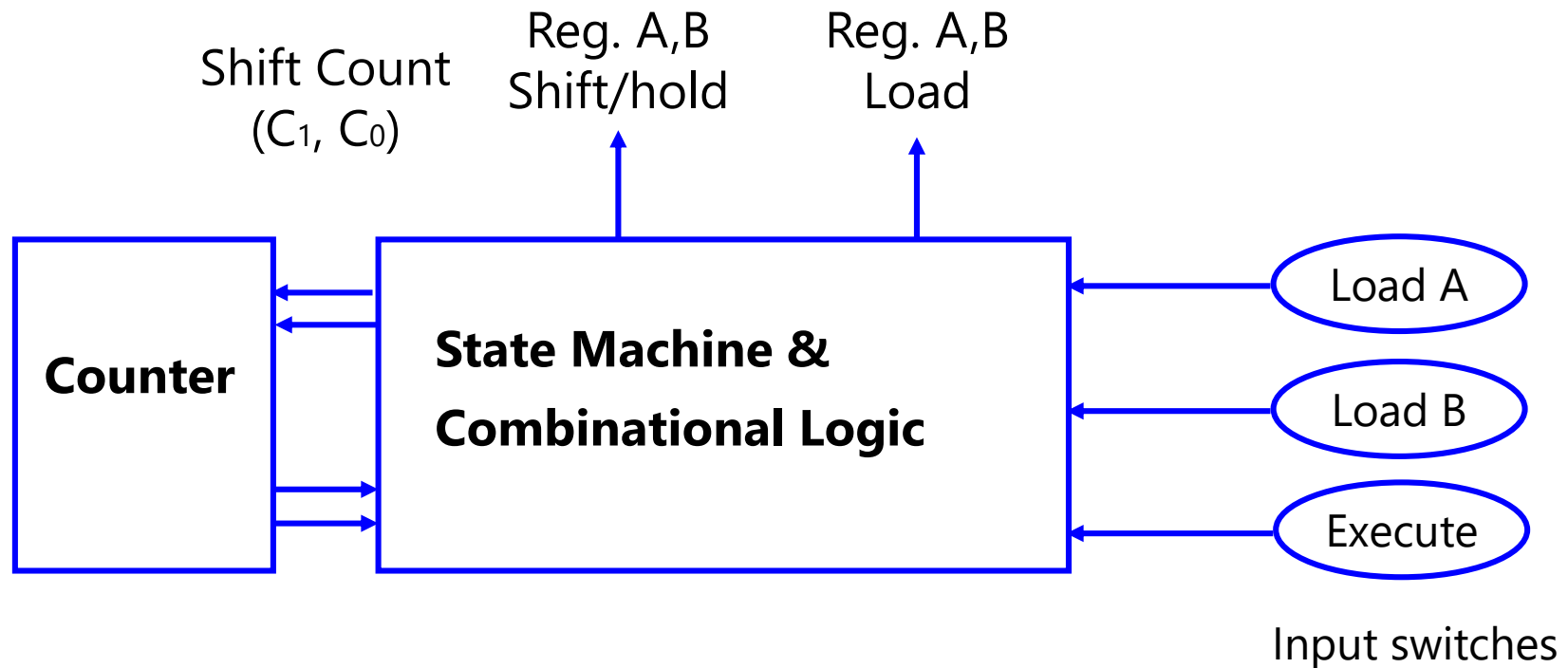
# Experiment 3 – Control Unit Block Diagram (Moore / Mealy)


 
## Experiment 3 – State Machine (Moore)

- Arcs are labeled with the counter outputs and the input Switch “EXECUTE” value
- Outputs are determined by only current state




You should include some capability to reset your controller (just involve running through once manually)

# Experiment 3 – State Machine
 
# Experiment 3 –State Machine (Mealy)

- Arcs are labeled with both inputs & outputs
- Fewer states than Moore machine (outputs depend on both state and inputs)



# Experiment 3 – State Machine



# Experiment 3 –State Machine (Mealy)

Exec. Switch ('E')	Q	C1	C0	Reg. Shift ( 'S' )	Q <sup>+</sup>	C1 <sup>+</sup>	C0 <sup>+</sup>
<b>0</b>	0	0	0	0	0	0	0
0	0	0	1	d	d	d	d
0	0	1	0	d	d	d	d
0	0	1	1	d	d	d	d
0	1	0	0	0	0	0	0
0	1	0	1	1	1	1	0
0	1	1	0	1	1	1	1
0	1	1	1	1	1	0	0
<b>1</b>	0	0	0	1	1	0	1
1	0	0	1	d	d	d	d
1	0	1	0	d	d	d	d
1	0	1	1	d	d	d	d
1	1	0	0	0	1	0	0
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	1	1	0	0

# State Machine Encoding

- Mealy and Moore machines are only one aspect of state machine design
- State encoding method is also important, 3 typical methods:
  - Binary numerical (easiest to think about, fewest registers)
  - Gray encoding (minimizes bit transitions when switching states)
  - One-hot encoding (minimizes decoding/next state circuitry, can use to efficiently implement lab 3...how?)

## Experiment 3 – Hints

- Make design modular and unit test (note how demo points are distributed)
- Do not gate clock (one inverter to shift clock edge is ok)
- Use flip-flops, counters, shift registers, to store state bit(s) in control unit (fully synchronous design)
- Use “don’t care” entries in state transition table to your advantage (the logic should not be very complicated)

## Experiment 3 – Demo Points

- Show correct loading of the A and B registers. (1 point)
- Show that the computation cycle is the right length. We will hit execute and hold it high. The shift registers should shift a total of 4 times. No more, no less. (1 point).
- Demonstrate the four routing operations. (1 point)
- Demonstrate the 8 functional operations. (1 point)
- Show that the computation cycle completes even if execute returns to 0 mid-computation. This will be clocked slowly (1 Hz), and execute will be switched high. As soon as it starts shifting, execute will be switched low. The circuit must complete its computation cycle as normal. (1 point)