

# **ECE 385**

Spring 2019

Experiment #6

## **Simple Computer SLC-3.2 in System Verilog**

Rob Audino and Soham Karanjikar

Section ABJ, Friday 2:00-4:50

TA: David Zhang

## **Introduction:**

In this lab, we were tasked with creating a simplified version of the LC-3 processor that we had learned about in ECE 120 and ECE 220. This simplified “SLC-3” was capable of less instructions than LC-3 but worked in a strikingly similar way. SLC-3 is essentially a 16-bit processor that performs three operations: fetch, decode, and execute. The fetch stage involved retrieving the desired instruction, whereas the decode stage determined what should be done given the desired instruction. Lastly, the execute function simply performed all of the details of the desired operation. In order to accomplish the task of building the SLC-3, we needed 3 ‘components’: memory, a CPU, and MEM2IO to facilitate data movement between the former two.

## **Written Description and Diagrams of SLC-3:**

As we described earlier, SLC-3 is a simplified, stripped down version of LC-3, and it has less operations. Although SLC-3 is missing the STI, LDI, LEA, JSRR, RTI, LD, TRAP, RET, and ST operations, it does add a PAUSE state.

The Fetch-Decode-Execute cycle obviously begins with Fetch, where the operation is actually retrieved. The Fetch operation itself begins with PC being loaded into MAR, after which MDR is loaded with the contents of the address that was specified by MAR. Next, the contents of MDR are stored into IR, and PC is then incremented by 1.

The next step in the cycle is decode. This step involves the ISDU selecting what the output signals become based on the contents of IR. The decode step is followed by the execute step, where the actual intentions of the instruction are carried out. Depending on the output of the decode step, different parts of the processor choose whether or not to operate and if they do operate, select what to output. The outputs of the individual active parts of the processor combine into a single output signal that is sent to the MEM2IO component. From there, MEM2IO will use inputs from the ISDU in order to select what exactly to do with the output.

The inputs of SLC come from the FPGA board, which include the reset, run, and continue buttons as well as the sixteen switches. The outputs of the SLC are the four hexadecimal displays and twelve LED’s on the FPGA board. During the operation of SLC, if Pause is pressed at any given time, the LED’s will illuminate with whatever is in IR, and will stay on until the continue button is pressed.

### Written Description of all .sv Modules:

Module: ALU

Inputs: [15:0] A, [15:0] B, ALUK

Outputs: [15:0] dout

Description: Accepts two data inputs and does one of four operations on the two : AND, ADD, NOT, PASSA.

Purpose: This is a key component that is used in various instructions in the LC3. It does the basic operations required for a processor to work.

Module: tristate

Inputs: Clk, tristate\_output\_enable, [15:0] Data\_write

Outputs: [15:0] Data\_read

Description: This component takes an input and a signal that allows the output to be HI-Z or the input.

Purpose: This allows us to not have a 0 or 1 but rather a NOINPUT. This means that we can have inputs to the bus that don't matter for the current state.

Module: slc3

Inputs: [15:0] S, Clk, Reset, Run, Continue

Outputs: [11:0] LED, [6:0] HEX0, [6:0] HEX1, [6:0] HEX2, [6:0] HEX3, [6:0] HEX4, [6:0] HEX5, [6:0] HEX6, [6:0] HEX7, CE, UB, LB, OE, WE, [19:0] ADDR

Description: This module incorporates everything that we did in the SLC3, this is the main component.

Purpose: It is instantiated by the toplevel to run the processor and use its functions.

Module: memory\_parser

Inputs: none

Outputs: none

Description: Given to us.

Purpose: Parses memory accordingly.

Module: MEM2IO

Inputs: Clk, Reset, [19:0] ADDR, CE, UB, LB, OE, WE, [15:0] Switches, [15:0] Data\_from\_CPU, [15:0] Data\_from\_SRAM

Outputs: [15:0] Data\_to\_CPU, [15:0] Data\_to\_SRAM, [3:0] HEX0, [3:0] HEX1, [3:0] HEX2, [3:0] HEX3

Description: Given to us. This makes memory from RAM available to us to work with.

Purpose: This allows us to work with memory and change its values. The creates a functionality between switches, buttons, hex displays and CPU. Just puts everything into the right place.

Module: lab6\_toplevel

Inputs: [15:0] S, Clk, Reset, Run, Continue

Outputs: [11:0] LED, CE, UB, LB, OE, WE, [19:0] ADDR, [6:0] HEX0, [6:0] HEX1, [6:0] HEX2, [6:0] HEX3, [6:0] HEX4, [6:0] HEX5, [6:0] HEX6, [6:0] HEX7

Description: Top level file of the project.

Purpose: This instantiates a SCL3 module and runs the processor and its functions.

Module: HexDriver

Inputs: [3:0] In0

Outputs: [3:0] Out0

Description: Takes inputs to drive HEXLEDS.

Purpose: Drives the Hex Displays that displays the outputs of the thing we want. Without this the Hex Displays would display random stuff or just not work.

Module: testbench

Inputs: none

Outputs: none

Description: Testing place to debug circuit and watch how waves change.

Purpose: To debug and simulate the processor.

Module: mux\_PC

Inputs: [15:0] A, [15:0] B, [15:0] C, [1:0] S

Outputs: [15:0] Out

Description: Mux that takes in 3 PC inputs from different paths to send the correct one to the bus.

Purpose: So that the correct PC value is sent into bus and there is no mismatch of what we want to do vs. what actually happens.

Module: mux\_MDR

Inputs: [15:0] A, [15:0] B, S,

Outputs: [15:0] Out

Description: MUX for the MDR so we can choose what goes into the MDR.

Purpose: So that the correct value passes through and not some other input we don't want.

Module: mux\_GATES

Inputs: [15:0] A, [15:0] B, [15:0] C, [15:0] D, [3:0] S

Outputs: [15:0] Out

Description: This mux controls what goes into the BUS from one of 4 inputs.

Purpose: This makes sure that only one thing is going to bus at a time and its correct. So if we want PC from the BUS, we will get that instead of some corrupted data.

Module: mux\_ADDR2

Inputs: [15:0] A, [15:0] B, [15:0] C, [15:0] D, [1:0] S

Outputs: [15:0] Out

Description: Mux for ADDR2 that takes in 4 inputs that are different sign extensions.  
Purpose: So that the correct value of which sign extend of IR we need is passed through instead of the wrong one.

Module: mux\_ADDR1

Inputs: [15:0] A, [15:0] B, S,

Outputs: [15:0] Out

Description: This takes in two inputs, either SR1 or PC and outputs the one we need.

Purpose: So that according to the signal sent to mux, we get the correct data we need and there is no mismatch.

Module: mux\_DR

Inputs: [2:0] A, S

Outputs: [2:0] Out

Description: Either takes 111 or IR[11:9] as an input and outputs correct one according to select signal.

Purpose: Same as other muxes. This allows us to use the correct value from SR2 that we need for the instruction to be carried out as necessary.

Module: mux\_SR1

Inputs: [2:0] A, [2:0] B, S

Outputs: [2:0] Out

Description: MUX for SR1, takes IR[11:9] and IR[8:6] as input and outputs what we need.

Purpose: Like the mux\_DR, this allows us to have the correct data picked at the correct time.

Module: mux\_SR2

Inputs: [15:0] A, [15:0] B, S

Outputs: [15:0] Out

Description: Takes sign extended IR and SR2OUT as inputs and correctly outputs according to signal.

Purpose: This allows us to pick the correct data at the correct time. Though all of these muxes could be converted into 1 module and be parameterized, we chose to do this to be more modular and straight forward.

Module: NZP

Inputs: Clk, NI, ZI, PI, LD\_CC

Outputs: NO, ZO, PO

Description: This does the logic of NZP from databus and outputs the correct NZP values.

Purpose: This allows us to SET\_CC and correctly perform operations that require it, such as BR.

Module: reg\_8

Inputs: Clk, Reset, Load, [7:0] D

Outputs: [7:0] Data\_Out

Description: This is a simple 8 bit register.

Purpose: Used in different cases, but mainly to test.

Module: reg\_4

Inputs: Clk, Reset, Load, [3:0] D

Outputs: [3:0] Data\_Out

Description: This is a simple 4 bit register.

Purpose: Though we did not use it thoroughly in the processor, it was used for testing and allowed us to see the intermediate values we wanted.

Module: reg\_16

Inputs: Clk, Reset, Load, [15:0] D

Outputs: [15:0] Data\_Out

Description: This is a simple 16 bit register.

Purpose: Used in different cases, but especially to create the 8 main registers R0-R7, IR etc.

Module: eightreg\_16

Inputs: Clk, Reset, Load, [15:0] D, [2:0] SR1IN, [2:0] SR2, [2:0] DRIN

Outputs: [15:0] SR1O, [15:0] SR2O

Description: This is a packed array of eight 16 bit registers

Purpose: This creates the eight registers R0-R7 into one module so they are all easily accessible in one component rather than having eight different 16 bit registers.

Module: flip\_flop

Inputs: Clk, Reset, Load, D

Outputs: Data\_Out

Description: Simple flip flop (1 bit register)

Purpose: Used to store value of Branch Enable.

Module: datapath

Inputs: LD\_MAR, LD\_MDR, LD\_IR, LD\_BEN, LD\_CC, LD\_REG, LD\_PC, LD\_LED, GatePC, GateMDR, GateALU, GateMARMUX, DRMUX, SR1MUX, SR2MUX, ADDR1MUX, MIO\_EN, [1:0] PCMUX, [1:0] ADDR2MUX, [1:0] ALUK, [15:0] MDR\_In

Outputs: BEN, [11:0] LED, [15:0] MAR, [15:0] MDR, [15:0] PC, [15:0] IR

Description: This module incorporates all of the muxes, registers, and buses into one so that the SLC3 does not have to instantiate all of those itself and can just use this one module.

Purpose: The main purpose of this in its most simple form is to output the correct data to the databus. However, there are multiple different components that go into this to make it possible. The most important part of this is that it picks which input to the gate\_mux we pick. This allows us to get the correct data we want, modified and tweaked to suit our needs.

Module: ISDU

Inputs: Clk, Reset, Run, Continue, IR\_5, IR\_11, BEN, [3:0] Opcode

Outputs: LD\_MAR, LD\_MDR, LD\_IR, LD\_BEN, LD\_CC, LD\_REG, LD\_PC, LD\_LED, GatePC, GateMDR, GateALU, GateMARMUX, DRMUX, SR1MUX, SR2MUX, ADDR1MUX, Mem\_CE, Mem\_UB, Mem\_LB, Mem\_OE, Mem\_WE, [1:0] PCMUX, [1:0] ADDR2MUX, [1:0] ALUK

Description: This is the state machine that controls the whole processor. It goes from one state to another depending on inputs and current state. It is a combination of the Moore and Mealy state machine. Based on the OPCODE, it goes to the correct states, and from there the processor knows what to execute. As a result, the data correctly flows through the data path to the BUS, and from there to memory.

Purpose: The list of Load signals, mux signals and enable signals, all go into the data path and the data is flows through correctly. Without this, nothing would be able to run, as the processor would not get signals to send to the data path, and either nothing would happen, or random values would be passed through the data bus into memory and we would get something we don't want. Along with datapath, this is another huge component of our SLC3.

The OPCODE, IR\_5, IR\_11 and BEN is how what state goes to what next state. What should happen in those states is written in the state description. That is where the signals below are written.

The outputs of this module are what control the whole processor.

GatePC, GateMDR, GateALU, GateMARMUX:

These are the signals to the Gate\_MUX and it controls which of the inputs (PC, MDR, ALU, ADDR1+ADDR2) are actually sent to databus. These are the 4 signals that control the main outputs of the datapath module.

DRMUX, SR1MUX, SR2MUX, ADDR1MUX, [1:0] PCMUX, [1:0] ADDR2MUX, [1:0] ALUK:

These are the signals that control the internal components (mainly muxes) of the datapath module. These internal components are used in order to create the data that is sent to the main outs (PC, MDR, ALU, ADDR1+ADDR2).

Mem\_CE, Mem\_UB, Mem\_LB, Mem\_OE, Mem\_WE:

These signals mainly interact with the MEM2IO module. These control the writes and reads from memory. This tells the datapath whether at the current state we want to store or fetch to complete the current instruction properly.

LD\_MAR, LD\_MDR, LD\_IR, LD\_BEN, LD\_CC, LD\_REG, LD\_PC, LD\_LED:

This picks where we want to store the correct data from the data bus. So if we want to Load MAR with current data, we keep all the other Loads off. This makes sure that no component is getting loaded with the data that isn't supposed to be in it.

There are 11 different main instructions which use all of these signals: ADD, ADDi, AND, ANDi, NOT, BR, JMP, JSR, STR, LDR, PAUSE. The details of what happens in each instructions and what states are hit can be seen in the state diagram. What happens in each state can be seen in our ISDU.sv file. It shows what signals are set in each state and what the next states are.

Screenshots:

```
124
125 // Assign next state
126 unique case (state)
127   Halted :
128     if (Run)
129       Next_state = S_18;
130   S_18 :
131     Next_state = S_33_1;
132   // Any states involving SRAM require more than one clock cycles.
133   // The exact number will be discussed in lecture.
134   S_33_1 :
135     Next_state = S_33_2;
136   S_33_2 :
137     Next_state = S_35;
138   S_35 :
139     Next_state = S_32;
140   // PauseIR1 and PauseIR2 are only for week 1 such that TAs can see
141   // the values in IR.
142   PauseIR1 :
143     if (Continue)
144       Next_state = PauseIR1;
145     else
146       Next_state = PauseIR2;
147   PauseIR2 :
148     if (Continue)
149       begin
150         Next_state = PauseIR2;
151       end
152     else
153       begin
154         Next_state = S_33;
```



```

153         begin
154             Next_state = S_32;
155         end
156     Pause1 :
157         if (~Continue)
158             Next_state = Pause1;
159         else
160             Next_state = Pause2;
161     Pause2 :
162         if (Continue)
163             begin //why do we have the begin here?
164                 Next_state = Pause2;
165             end
166         else
167             begin
168                 Next_state = S_18;
169             end
170     S_32 :
171         case (Opcode) //Different Operations/Instructions
172             4'b0001 :
173                 Next_state = S_01; //ADD
174             4'b0101 :
175                 Next_state = S_05; //AND
176             4'b1001 :
177                 Next_state = S_09; //NOT
178             4'b0000 :
179                 Next_state = S_00; //BR
180             4'b1100 :
181                 Next_state = S_12; //JMP
182             4'b0100 :
183                 Next_state = S_04; //JSR

```

```

180             4'b1100 :
181                 Next_state = S_12; //JMP
182             4'b0100 :
183                 Next_state = S_04; //JSR
184             4'b0110 :
185                 Next_state = S_06; //LDR
186             4'b0111 :
187                 Next_state = S_07; //STR
188             4'b1101 :
189                 Next_state = Pause1;
190         default :
191             Next_state = S_18;
192     endcase
193     S_01 : Next_state = S_18; //ADD
194     S_05 : Next_state = S_18; //AND
195     S_09 : Next_state = S_18; //NOT
196     S_06 : Next_state = S_25_1; //LDR
197     S_25_1 : Next_state = S_25_2;
198     S_25_2 : Next_state = S_27;
199     S_27 : Next_state = S_18;
200     S_07 : Next_state = S_23; //STR
201     S_23 : Next_state = S_16_1;
202     S_16_1 : Next_state = S_16_2;
203     S_16_2 : Next_state = S_18;
204     S_00 : //BR
205         if (BEN == 1'b1)
206             Next_state = S_22;
207         else
208             Next_state = S_18;
209     S_22 : Next_state = S_18;
210     S_12 : Next_state = S_18; //JMP

```

```

207         else
208             Next_state = S_18;
209         S_22 : Next_state = S_18;
210         S_12 : Next_state = S_18;           //JMP
211         S_04 : Next_state = S_21;           //JSR
212         S_21 : Next_state = S_18;
213         default : ;
214     endcase
215
216     // Assign control signals based on current state
217     case (State)
218     Halted: ;
219     S_18 :
220     begin
221         GatePC = 1'b1;
222         LD_MAR = 1'b1;
223         PCMUX = 2'b00;
224         LD_PC = 1'b1;
225     end
226     S_33_1 :
227     begin
228         Mem_OE = 1'b0; //mem_we removed
229     end
230     S_33_2 :
231     begin
232         Mem_OE = 1'b0; //mem_we removed
233         LD_MDR = 1'b1;
234     end
235     S_35 :
236     begin

```

```

234         LD_MDR = 1'b1;
235     end
236     S_35 :
237     begin
238         GateMDR = 1'b1;
239         LD_IR = 1'b1;
240     end
241     PauseIR1: ;
242     PauseIR2: ;
243     Pause1:
244     begin
245         LD_LED = 1'b1;
246     end
247     Pause2: ;
248     S_32 :
249     begin
250         LD_BEN = 1'b1;
251     end
252     S_01 : //ADD
253     begin
254         SR2MUX = IR_5;
255         SR1MUX = 1'b1;
256         ALUK = 2'b00;
257         GateALU = 1'b1;
258         LD_REG = 1'b1;
259         LD_CC = 1'b1;
260         // incomplete...
261     end
262     S_05 : //AND
263     begin
264         SR2MUX = IR_5;

```

```

261     end
262 s_05 : //AND
263     begin
264         SR2MUX = IR_5;
265         SR1MUX = 1'b1;
266         ALUK = 2'b01;
267         GateALU = 1'b1;
268         LD_REG = 1'b1;
269         LD_CC = 1'b1;
270     end
271 s_09 : //NOT
272     begin
273         SR2MUX = 1'b0; //added
274         SR1MUX = 1'b1;
275         ALUK = 2'b10;
276         GateALU = 1'b1;
277         LD_REG = 1'b1;
278         LD_CC = 1'b1;
279     end
280 s_00 :
281     begin
282         Mem_WE = 1'b1; //added
283         Mem_OE = 1'b1;
284     end
285 s_22 :
286     begin
287         ADDR1MUX = 1'b0;
288         ADDR2MUX = 2'b10;
289         PCMUX = 2'b10;
290         LD_PC = 1'b1;
291     end

```

```

288         ADDR2MUX = 2'b10;
289         PCMUX = 2'b10;
290         LD_PC = 1'b1;
291     end
292 s_12 : //JMP
293     begin
294         SR1MUX = 1'b1;
295         ADDR1MUX = 1'b1;
296         ADDR2MUX = 2'b00;
297         PCMUX = 2'b10;
298         LD_PC = 1'b1;
299     end
300 s_04 : //JSR
301     begin
302         GatePC = 1'b1;
303         DRMUX = IR_11;
304         LD_REG = 1'b1;
305     end
306 s_21 :
307     begin
308         ADDR1MUX = 1'b0;
309         ADDR2MUX = 2'b11;
310         PCMUX = 2'b10;
311         LD_PC = 1'b1;
312     end
313 s_06 : //LDR
314     begin
315         SR1MUX = 1'b1;
316         ADDR1MUX = 1'b1;
317         ADDR2MUX = 2'b01;
318         GatePC = 1'b1;

```

```

315         SRIMUX = 1'b1;
316         ADDR1MUX = 1'b1;
317         ADDR2MUX = 2'b01;
318         GateMARMUX = 1'b1;
319         LD_MAR = 1'b1;
320     end
321 S_25_1:
322     begin
323         Mem_WE = 1'b1;
324         Mem_OE = 1'b0;
325     end
326 S_25_2:
327     begin
328         Mem_OE = 1'b0;
329         Mem_WE = 1'b1;
330         LD_MDR = 1'b1;
331     end
332 S_27 :
333     begin
334         GateMDR = 1'b1;
335         LD_REG = 1'b1;
336         LD_CC = 1'b1;
337     end
338 S_07 :      //STR
339     begin
340         SRIMUX = 1'b1;
341         ADDR1MUX = 1'b1;
342         ADDR2MUX = 2'b01;
343         GateMARMUX = 1'b1;
344         LD_MAR = 1'b1;
345     end

```


```

333     begin
334         GateMDR = 1'b1;
335         LD_REG = 1'b1;
336         LD_CC = 1'b1;
337     end
338 S_07 :      //STR
339     begin
340         SRIMUX = 1'b1;
341         ADDR1MUX = 1'b1;
342         ADDR2MUX = 2'b01;
343         GateMARMUX = 1'b1;
344         LD_MAR = 1'b1;
345     end
346 S_23 :
347     begin
348         SRIMUX = 1'b0;
349         ALUK = 2'b11;
350         GateALU = 1'b1;
351         LD_MDR = 1'b1;
352     end
353 S_16_1 :
354     begin
355         Mem_OE = 1'b1;
356         Mem_WE = 1'b0;
357     end
358 S_16_2 :
359     begin
360         Mem_OE = 1'b1;
361         Mem_WE = 1'b0;
362     end
363 // You need to finish the rest of states

```
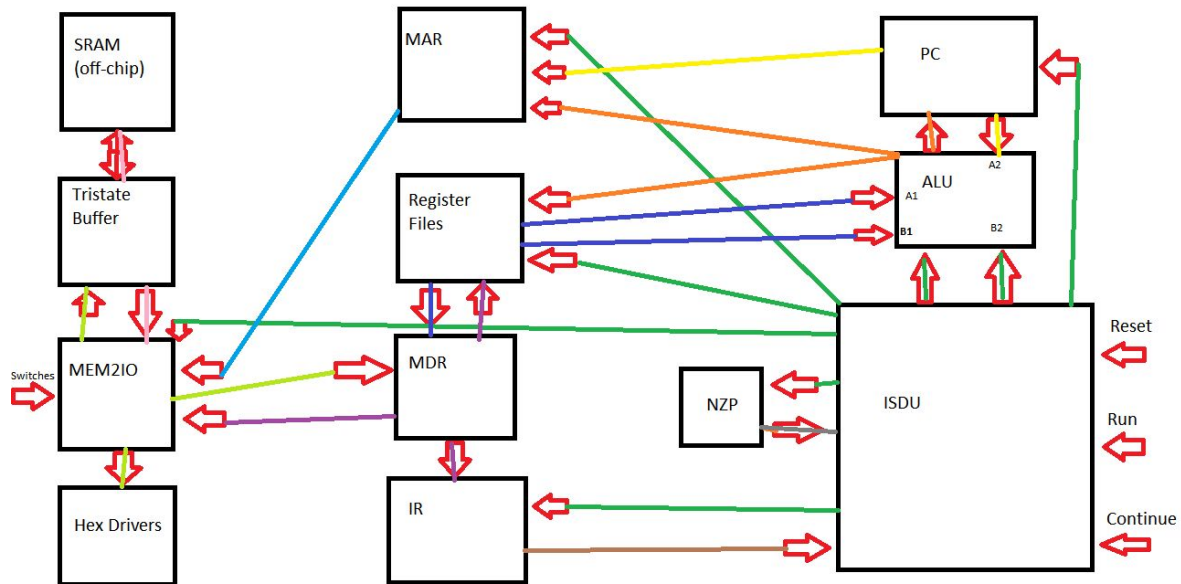
### Block Diagram of slc3.sv:


❑ This diagram should represent the placement of all your modules in the slc3.sv. Please only include the slc3.sv diagram and not the RTL view of every module.



### Description of the operation of the ISDU (Instruction Sequence Decoder Unit):


Combined with description/purpose

## State Diagram of ISDU:

 



## Simulations of SLC-3 Instructions:

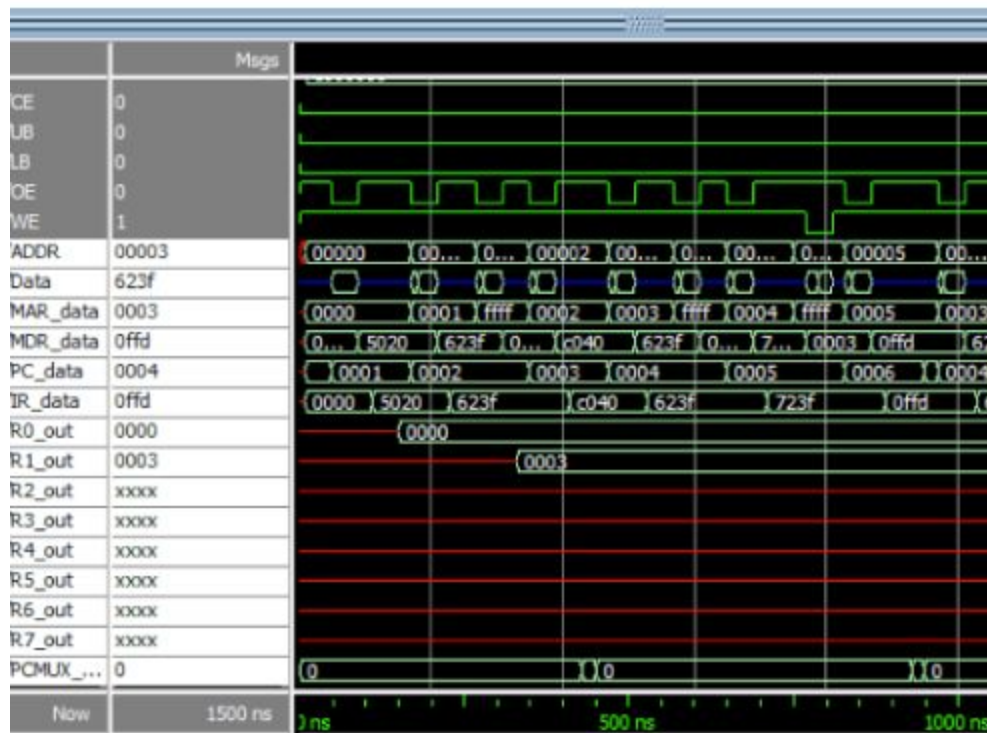

The three instructions visible in the image above are ANDi, LDR and JMP. Further the changing of MDR scrolling through memory is also visible.

ANDi is the first instruction that executes at 150ns. SR=R0, DR=R0, IMM5 = #0. This puts 0000 into R0.

LDR is the second instruction that executes. This occurs at 275ns. DR = R1, BaseR = R0, Offset = #-1. This puts the value stored in Memory address [R0 + -1] into R1.

Finally, the third instruction that occurs is JMP at 350ns. BaseR = R1. This puts whatever is in R1 into PC. So PC becomes 0003.

## Post-Lab Questions:

1. Q: Fill in the table shown in 5.6 with your design's statistics

A:

LUT	593
DSP	0
BRAM	0
Flip-Flop	280
Frequency	94.47 MHz
Static Power	98.47 mW
Dynamic Power	0
Total Power	179.29 mW

2. Q: What is the function of the MEM2IO.sv module?

A: MEM2IO essentially functions as a moderator for the connections between memory, the CPU, the hex displays, and the switches. If the write enable signal is high, MEM2IO will write the received data into the hex drivers. However, if the read enable signal is high, and MEM2IO receives the address of an I/O device, then it will read the data input from the switches directly.

3. Q: What is the difference between the BR and JMP instructions?

A: The first major difference between the BR and JMP instructions is that JMP is an unconditional jump, whereas BR will only jump if the stated condition codes are matching. Secondly, the jump for BR is specified in the offset inside of the 16 bit instruction and starts from the current PC, whereas the jump for JMP is to whatever address is inside of BaseR.

4. Q: What is the purpose of the R signal in Patt and Patel? How do we compensate for the lack of the signal in our design? What implications does this have for synchronization?

A: The R signal lets us know if a fetch from memory has been completed properly: if so, then we proceed to the next state. If not, it simply loops. The way we did it is as follows: we knew that it would not take an infinite number of cycles to fetch, so we just set it to a finite number. To do so, we account for it by the number of states we have for instructions which requires a fetch operation to be completed from memory. We just add an extra state whenever we need to read enable.



## Conclusion:

Overall, Lab 6 was far and away the most difficult, time consuming, and tedious lab we've worked on so far. The fact that it was a two week lab was sort of unassuming: week one didn't require much work, but it needed to be spent understanding the datapath and the ISDU so that we could get part two working the following week. While many students created the entire datapath week one, we decided to do the bare minimum and just create the sections required for week one: namely, the ones required for the fetch operation. We received all of the points week one and went into week two not understanding how much work was necessary. The majority of the time we spent debugging concerned two issues: the ISDU and which inputs and outputs to include for each of the modules. After doing some experimenting, we eventually decided what inputs were necessary for each of the modules, and we moved on to the ISDU.

We began to go through the test programs for the lab. Thankfully, the test programs were created so that you could figure out which operations worked and which ones didn't. Our program passed the two Basic I/O tests and the XOR tests, but kept on failing the Self-Modifying code test. We scanned desperately through our ISDU file and eventually figured out that we had misplaced the Write Enable signal into states 33\_1 and 33\_2, and forgotten to include it in state 0 (the branch state). After correcting this, we were able to successfully perform both the Self-Modifying and Multiplication tests, but we were still having issues with the Bubble Sort test. Thankfully, we found out from another student that we were actually performing the test incorrectly, and once he did the test the correct way, our Bubble Sort actually worked.

In retrospect, this was a very challenging, but rewarding lab. We had to work so much out by ourselves and decipher the code that was given to us. The lab instructions weren't as clear as we would have liked, so we had to figure a lot out for ourselves, especially when it came to MEM2IO and the ISDU, so I think it would be helpful in upcoming semesters for the lab instructions to be a bit more thorough. If we could change something about the lab, we would have the workload split up more evenly between the two weeks; however, with there only being three phases in the fetch-decode-execute cycle, I can see why the course staff has organized it the way they have.